

Ring and Johnson Counters

CASEST



हैदराबाद विश्वविद्यालय
University of Hyderabad

Lab Report No. 9

MV407: IC Design Lab-1 (Digital)

Submitted by:

Full Name	Enrollment No.
-----------	----------------

Abhinav M	23PMMT11(@uohyd.ac.in)
-----------	------------------------

Lab Instructor: Dr. Bhawna Gomber

Teaching Assistant: Ms. Bhargavi

Center for Advanced Studies in Electronics Science and Technology
University of Hyderabad
Hyderabad, India
December 16, 2023

Contents

1	Ring counter	1
1.1	Objective	1
1.2	Code	1
1.3	Elaborated design	2
1.4	Timing diagram	2
1.5	Remarks	2
2	Johnson counter	3
2.1	Objective	3
2.2	Code	3
2.3	Elaborated design	4
2.4	Timing diagram	4
2.5	Remarks	4
3	References	5
A	Appendix A: GitHub Repo	6



1 | Ring counter

1.1 | Objective

Design RTL for ring counter. Verify its functionality using testbench.

1.2 | Code

1.2.1 | Design

```
1
2 `timescale 1ns / 1ps
3 ///////////////////////////////////////////////////////////////////
4 // Company : CASEST, University of Hyderabad:
5 // Author : Abhinav M
6 //
7 // Create Date: 10/25/2023 02:52:37 PM
8 // Design Name:
9 // Module Name: CB_DFF_async
10 // Project Name:
11 // Target Devices:
12 // Tool Versions:
13 // Description:
14 //
15 // Dependencies:
16 //
17 // Revision:
18 // Revision 0.01 - File Created
19 // Additional Comments:
20 //
21 ///////////////////////////////////////////////////////////////////
22 module ringcounter (out,clk,rst);
23 input clk,rst;
24 output [3:0] out;
25 reg [3:0] q;
26
27 always @(posedge clk) begin
28 if(rst) begin
29 q <= 4'b1000;
30 end
31 else begin
32 q[0] <= q[3];
33 q[1] <= q[0];
34 q[2] <= q[1];
35 q[3] <= q[2];
36 end
37 end
38
39 assign out = q;
40 endmodule
```

1.2.2 | Testbench

```
1
2 `timescale 1ns / 1ps
3 ///////////////////////////////////////////////////////////////////
4 // Company:
5 // Author: Abhinav M
6 //
7 // Create Date: 10/25/2023 03:02:13 PM
8 // Design Name:
9 // Module Name: tb_CB_DFF_sync
10 // Project Name:
11 // Target Devices:
12 // Tool Versions:
13 // Description:
14 //
15 // Dependencies:
16 //
17 // Revision:
18 // Revision 0.01 - File Created
19 // Additional Comments:
20 //
21 ///////////////////////////////////////////////////////////////////
22 module ringcounter_tb ();
23 reg clk,rst;
24 wire [3:0] out;
25
26 ringcounter uut(out,clk,rst);
27
```

```

28 initial begin
29   clk = 0;
30   forever #5 clk = ~clk;
31 end
32
33 initial begin
34   rst = 1'b1;
35   #20 rst = 1'b0;
36   #200 $ finish;
37 end
38 endmodule

```

1.3 | Elaborated design

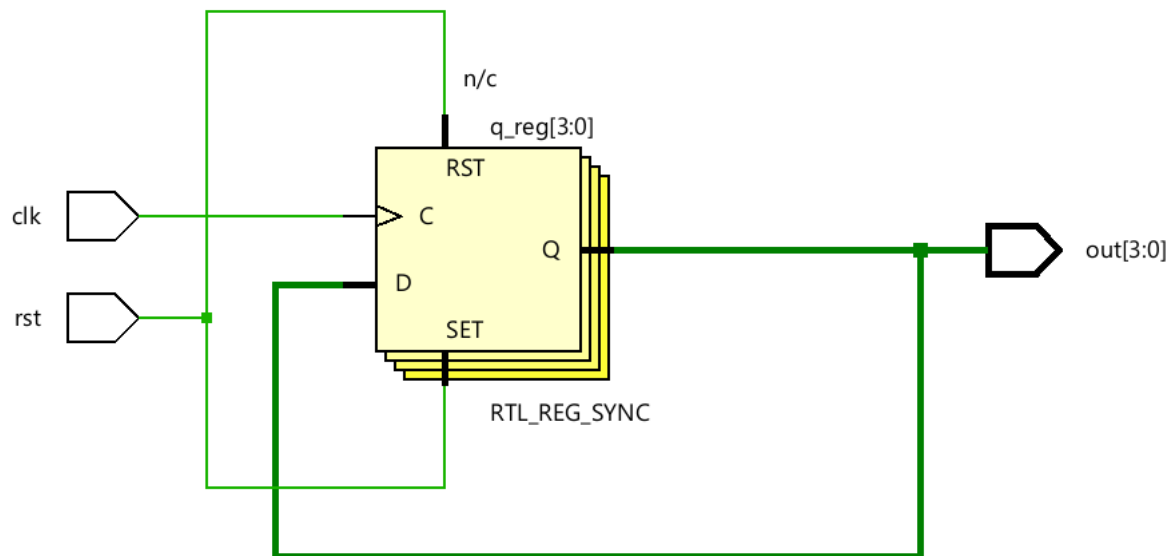


Figure 1.1: Elaborated design

1.4 | Timing diagram

 


Figure 1.2: Timing diagram

1.5 | Remarks

Circuit was designed and tested successfully, expected functionality was achieved.



2 | Johnson counter

2.1 | Objective

Design RTL for johnson counter. Verify its functionality using testbench.

2.2 | Code

2.2.1 | Design

```
1
2 `timescale 1ns / 1ps
3 ///////////////////////////////////////////////////////////////////
4 // Company : CASEST, University of Hyderabad:
5 // Author : Abhinav M
6 //
7 // Create Date: 10/25/2023 02:52:37 PM
8 // Design Name:
9 // Module Name: CB_DFF_async
10 // Project Name:
11 // Target Devices:
12 // Tool Versions:
13 // Description:
14 //
15 // Dependencies:
16 //
17 // Revision:
18 // Revision 0.01 - File Created
19 // Additional Comments:
20 //
21 ///////////////////////////////////////////////////////////////////
22 module johnsoncounter (out,clk,rst);
23 input clk,rst;
24 output [3:0] out;
25 reg [3:0] q;
26
27 always @(posedge clk) begin
28 if(rst) begin
29 q <= 4'b1000;
30 end
31 else begin
32 q[3] <= q[0];
33 q[2] <= q[3];
34 q[1] <= q[2];
35 q[0] <= q[1];
36 end
37 end
38
39 assign out = q;
40 endmodule
```

2.2.2 | Testbench

```
1
2 `timescale 1ns / 1ps
3 ///////////////////////////////////////////////////////////////////
4 // Company:
5 // Author: Abhinav M
6 //
7 // Create Date: 10/25/2023 03:02:13 PM
8 // Design Name:
9 // Module Name: tb_CB_DFF_sync
10 // Project Name:
11 // Target Devices:
12 // Tool Versions:
13 // Description:
14 //
15 // Dependencies:
16 //
17 // Revision:
18 // Revision 0.01 - File Created
19 // Additional Comments:
20 //
21 ///////////////////////////////////////////////////////////////////
22 module johnsoncounter_tb ();
23 reg clk,rst;
24 wire [3:0] out;
25
26 johnsoncounter uut(out,clk,rst);
27
```

```

28 | initial begin
29 |   clk = 0;
30 |   forever #5 clk = ~clk;
31 | end
32 |
33 | initial begin
34 |   rst = 1'b1;
35 |   #20 rst = 1'b0;
36 |   #200 $ finish;
37 | end
38 | endmodule

```

2.3 | Elaborated design

 


Figure 2.1: Elaborated design

2.4 | Timing diagram

 


Figure 2.2: Timing diagram

2.5 | Remarks

Circuit was designed and tested successfully, expected functionality was achieved.



3 | References



A | Appendix A: GitHub Repo

The GitHub repo referenced below contains the Verilog code and testbenches mentioned in this report.

<https://github.com/AbhinavM2000/MV401D/>