

# Realizing Multiplexers and Comparators in structural and RTL Verilog

## CASEST



हैदराबाद विश्वविद्यालय  
University of Hyderabad

Lab Report No. 2

MV407: IC Design Lab-1 (Digital)

Submitted by:

Full Name	Enrollment No.
-----------	----------------

Abhinav M	23PMMT11(@uohyd.ac.in)
-----------	------------------------

Lab Instructor: Dr. Bhawna Gomber

Teaching Assistant: Ms. Bhargavi


Center for Advanced Studies in Electronics Science and Technology  
University of Hyderabad  
Hyderabad, India  
October 4, 2023

# Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
<b>2</b>	<b>4 bit 2:1 Multiplexer</b>	<b>1</b>
2.1	Objectives . . . . .	1
2.2	Schematic . . . . .	1
2.3	Truth table . . . . .	2
2.4	Code . . . . .	2
2.5	Elaborated design . . . . .	4
2.6	Timing diagram . . . . .	5
2.7	Utilization summary . . . . .	5
2.8	Remarks . . . . .	6
<b>3</b>	<b>4bit, 4:1 Multiplexer by instantiating 2:1 MUX</b>	<b>7</b>
3.1	Objectives . . . . .	7
3.2	Schematic . . . . .	7
3.3	Truth table . . . . .	7
3.4	Code . . . . .	7
3.5	Elaborated design . . . . .	10
3.6	Elaborated design . . . . .	10
3.7	Timing diagram . . . . .	10
3.8	Utilization summary . . . . .	11
3.9	Remarks . . . . .	11
<b>4</b>	<b>4 bit 8:1 Multiplexer by instantiating 4:1, 2:1 MUXs</b>	<b>12</b>
4.1	Objectives . . . . .	12
4.2	Schematic . . . . .	12
4.3	Truth table . . . . .	12
4.4	Code . . . . .	13
4.5	Elaborated design . . . . .	14
4.6	Timing diagram . . . . .	14
4.7	Utilization summary . . . . .	14
4.8	Remarks . . . . .	15
<b>5</b>	<b>1 bit comparator</b>	<b>16</b>
5.1	Objectives . . . . .	16
5.2	Schematic . . . . .	16
5.3	Truth table . . . . .	16
5.4	Code . . . . .	16
5.5	Elaborated design . . . . .	18
5.6	Timing diagram . . . . .	19
5.7	Utilization summary . . . . .	20
5.8	Remarks . . . . .	20
<b>6</b>	<b>4 bit comparator using 1 bit comparator</b>	<b>21</b>
6.1	Objectives . . . . .	21
6.2	Logic . . . . .	21
6.3	Code . . . . .	21
6.4	Elaborated design . . . . .	22
6.5	Timing diagram . . . . .	23
6.6	Utilization summary . . . . .	23
6.7	Remarks . . . . .	23
<b>7</b>	<b>References</b>	<b>24</b>
<b>A</b>	<b>Appendix A: GitHub Repo</b>	<b>25</b>

## 1 | Introduction

This lab report details the implementation of comparators and multiplexers in Verilog Hardware Description Language (HDL) in structural and Register Transfer Level (RTL) / Dataflow paradigms. The code was written and synthesized on Xilinx Vivado v2020 on a Zynq 7000 xc7c020clg484-1 platform with 53200 Look Up Tables (LUTs) and 400 Input Output Blocks (IOBs). This report is a part of the MV407 course at CASEST, University of Hyderabad (2023).

 

**Figure 1.1:** Zedboard: A common FPGA platform powered by the Zynq 7000 family.

## 2 | 4 bit 2:1 Multiplexer


04-10-2023

### 2.1 | Objectives

- To design a 4 bit, 2:1 Multiplexer using structural and RTL Verilog and verify its functionality using a testbench.

### 2.2 | Schematic

4 bit 2x1 mux works in the same way as its 1 bit counterpart only difference being that the inputs and hence output will be 4 bit words. Fig 2.1 shows the block diagram where  $A_0$  and  $A_1$  are 4-bits each.

 

**Figure 2.1:** Block diagram of the 2:1 MUX.



## 2.3 Truth table

The truth table can be used to derive the Boolean expression:

Input 1	Input 2	S (Select)	Y (Output)
$A_0$	$A_1$	0	$A_0$
$A_0$	$A_1$	1	$A_1$

## 2.4 Code

### 2.4.1 Structural Design

```
1  `timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Company: CASEST, University of Hyderabad
4  // Author: Abhinav M
5  //
6  // Create Date: 28.09.2023 07:30:18
7  // Design Name:
8  // Module Name: BS_4_MUX21
9  // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22
23 module BS_4_MUX21(output [3:0]data,input s,input [3:0]a,b);
24
25 mux_2_1 m[3:0](s,a,b,data); //used 1 bit 2x1 mux to make 4 bit 2x1 mux
26
27 endmodule
```

### 2.4.2 Testbench

```
1  `timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Company: CASEST, University of Hyderabad
4  // Author: Abhinav M
5  //
6  // Create Date: 01.10.2023 22:50:56
7  // Design Name:
8  // Module Name: tb_BS_4_MUX21
9  // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22
23 module tb_BS_4_MUX21();
24 wire [3:0] data;
25 reg s;
26 reg [0:3]a,b;
27 BS_4_MUX21 uut(data,s,a,b);
28
29 initial
30 begin
31
32     a=4'b0001;b=4'b1111;
33     s=1'b0;
34     #10 s=1'b1;
35
36
37     #10 $finish;
38 end
```



```
39  
40  
41 endmodule
```

### 2.4.3 | RTL Design

```
1  `timescale 1ns / 1ps  
2  ///////////////////////////////////////////////////////////////////  
3  // Company: CASEST, University of Hyderabad  
4  // Author: Abhinav M  
5  //  
6  // Create Date: 28.09.2023 07:30:46  
7  // Design Name:  
8  // Module Name: BR_4_MUX21  
9  // Project Name:  
10 // Target Devices:  
11 // Tool Versions:  
12 // Description:  
13 //  
14 // Dependencies:  
15 //  
16 // Revision:  
17 // Revision 0.01 - File Created  
18 // Additional Comments:  
19 //  
20 ///////////////////////////////////////////////////////////////////  
21  
22  
23 module BR_4_MUX21(output [3:0]data,input s,input [3:0]a,b);  
24  
25     assign data=s?a:b;  
26  
27 endmodule
```


### 2.4.4 | Testbench

```
1  `timescale 1ns / 1ps  
2  ///////////////////////////////////////////////////////////////////  
3  // Company: CASEST, University of Hyderabad  
4  // Author: Abhinav M  
5  //  
6  // Create Date: 01.10.2023 22:18:47  
7  // Design Name:  
8  // Module Name: tb_BR_4_MUX21  
9  // Project Name:  
10 // Target Devices:  
11 // Tool Versions:  
12 // Description:  
13 //  
14 // Dependencies:  
15 //  
16 // Revision:  
17 // Revision 0.01 - File Created  
18 // Additional Comments:  
19 //  
20 ///////////////////////////////////////////////////////////////////  
21  
22  
23 module tb_BR_4_MUX21();  
24 wire [0:3]data;  
25 reg s;  
26 reg [0:3]a,b;  
27 BR_4_MUX21 uut(data, s,a,b);  
28  
29     initial  
30     begin  
31  
32         a=4'b0001;b=4'b1000;  
33  
34         s=1;  
35         #10 s=0;  
36  
37         #10 $finish;  
38     end  
39  
40  
41 endmodule
```




## 2.5 | Elaborated design

### 2.5.1 | Structural

 

**Figure 2.2:** Elaborated design of 4 bit 2x1 mux using 1 bit 2x1 muxes.

### 2.5.2 | RTL

 


**Figure 2.3:** Elaborated design of 4 bit 2x1 mux in RTL style.




## 2.6 | Timing diagram

### 2.6.1 | Structural

 

**Figure 2.4:** Timing diagram of the 4 bit 2x1 mux obtained after simulating the testbench.


### 2.6.2 | RTL

 

**Figure 2.5:** Timing diagram of the 4 bit 2x1 mux obtained after simulating the testbench.


## 2.7 | Utilization summary

### 2.7.1 | Structural

 

**Figure 2.6:** Resource utilization summary of the synthesized design.

### 2.7.2 | RTL

 

**Figure 2.7:** Resource utilization summary of the synthesized design.



### 2.8 | Remarks

The design and testing of 4 bit 2x1 mux in structural (using 1 bit 2x1 mux) and RTL Verilog has been carried out. The device is showing expected behaviour.




### 3 | 4bit, 4:1 Multiplexer by instantiating 2:1 MUX

04-10-2023

#### 3.1 | Objectives

- To use the designed multiplexer in 2 to design a 4bit, 4:1 Multiplexer by instantiating as well as RTL and verify its functionality using a testbench.

#### 3.2 | Schematic

 

**Figure 3.1:** Block diagram of the full adder.

#### 3.3 | Truth table

The truth table of the 4x1 mux is shown below.

Input 1	Input 2	Input 3	Input 4	$S_0$	$S_1$	Y (Output)
$A_0$	$A_1$	$A_2$	$A_3$	0	0	$A_0$
$A_0$	$A_1$	$A_2$	$A_3$	0	1	$A_1$
$A_0$	$A_1$	$A_2$	$A_3$	1	0	$A_2$
$A_0$	$A_1$	$A_2$	$A_3$	1	1	$A_3$

**Table 3.1:** Truth table for the 4x1 mux.

#### 3.4 | Code

##### 3.4.1 | Structural Design

```

1  `timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Company: CASEST, University of Hyderabad
4  // Author: Abhinav M
5  //
6  // Create Date: 01.10.2023 19:36:17
7  // Design Name:
8  // Module Name: BS_4_MUX_41
9  // Project Name:
10 // Target Devices:

```



```
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////
21
22 module BS_4_MUX41(output [3:0]y,input s0, s1,input [3:0]A0,A1,A2,A3);
23
24     wire [3:0]y0, y1;
25     BR_4_MUX21 m1(y1,s1, A2, A3);
26     BR_4_MUX21 m2(y0, s1, A0,A1);
27     BR_4_MUX21 m3(y, s0, y0,y1);
28
29
30 endmodule
```

### 3.4.2 | Testbench

```
1 `timescale 1ns / 1ps
2 ///////////////////////////////////////////////////
3 // Company: CASEST, University of Hyderabad
4 // Author: Abhinav M
5 //
6 // Create Date: 01.10.2023 22:23:57
7 // Design Name:
8 // Module Name: tb_BS_4_MUX41
9 // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////
21
22 module tb_BS_4_MUX41();
23     reg s0,s1;
24     reg [3:0]A0,A1,A2,A3;
25     wire [3:0]data;
26     BS_4_MUX41 uut(data,s0,s1,A0,A1,A2,A3);
27     initial
28     begin
29
30         A0=4'b0001;A1=4'b0010;A2=4'b0100;A3=4'b1000;
31         s0=0;s1=0;
32         #10 s0=0;s1=1;
33         #10 s0=1;s1=0;
34         #10 s0=1;s1=1;
35         #10 $finish;
36     end
37
38 endmodule
```

### 3.4.3 | RTL Design

```
1 `timescale 1ns / 1ps
2 ///////////////////////////////////////////////////
3 // Company: CASEST, University of Hyderabad
4 // Author: Abhinav M
5 //
6 // Create Date: 01.10.2023 15:01:41
7 // Design Name:
8 // Module Name: BR_4_MUX_41
9 // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
```




```
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22
23 module BR_4_MUX_41(output [3:0]data,input [1:0]s,input [3:0]A0,A1,A2,A3);
24
25 assign data = (s==2'b00)?A0:
26             (s == 2'b01) ? A1 :
27             (s == 2'b10) ? A2 :
28             (s == 2'b11) ? A3 :
29             2'b00;
30
31 endmodule
```

### 3.4.4 | Testbench

```
1  `timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Company: CASEST, University of Hyderabad
4  // Author: Abhinav M
5  //
6  // Create Date: 01.10.2023 19:12:50
7  // Design Name:
8  // Module Name: tb_BR_4_MUX_41
9  // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22
23 module tb_BR_4_MUX_41();
24 reg [1:0]s;
25 reg [3:0]A0,A1,A2,A3;
26 wire [3:0]data;
27 BR_4_MUX_41 uut(data,s,A0,A1,A2,A3);
28 initial
29 begin
30
31     #10 A0=4'b0001;A1=4'b0010;A2=4'b0100;A3=4'b1000;
32     #10 s=2'b00;
33     #10 s=2'b01;
34     #10 s=2'b10;
35     #10 s=2'b11;
36
37
38
39
40     #10 $finish;
41 end
42
43
44
45 endmodule
```

## 3.5 | Elaborated design


### 3.5.1 | Structural

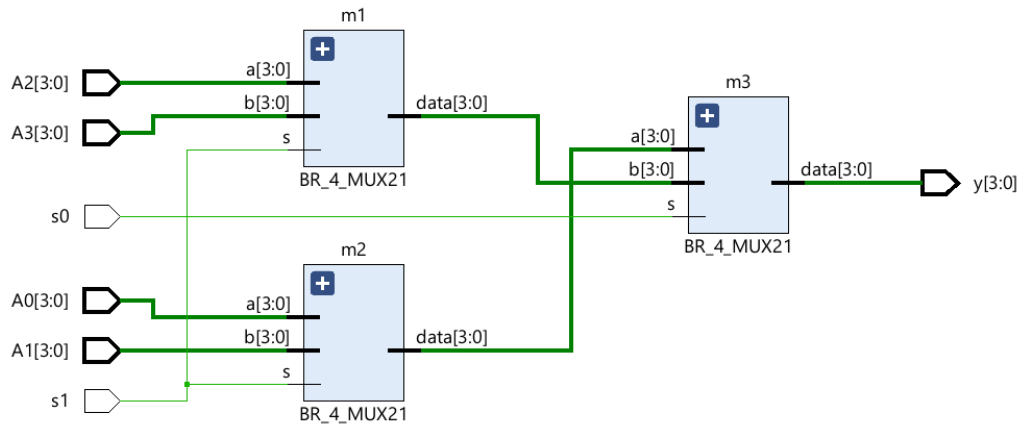

**Figure 3.2:** Elaborated design of the 4 bit 4x1 mux using three 4 bit 2x1 muxes.

## 3.6 | Elaborated design


### 3.6.1 | RTL

 

**Figure 3.3:** Elaborated design of the 4 bit 4x1 mux in RTL style.

## 3.7 | Timing diagram


### 3.7.1 | Structural

 

**Figure 3.4:** Timing diagram of the 4 bit 4x1 mux obtained after simulating the testbench.



### 3.7.2 | RTL

 


**Figure 3.5:** Timing diagram of the 4 bit 4x1 mux obtained after simulating the testbench.

## 3.8 | Utilization summary

### 3.8.1 | Structural


Resource	Utilization	Available	Utilization %
LUT	4	53200	0.01
IO	22	200	11.00

 

**Figure 3.6:** Resource utilization summary of the synthesized design.

### 3.8.2 | RTL

Resource	Utilization	Available	Utilization %
LUT	4	53200	0.01
IO	22	200	11.00

 

**Figure 3.7:** Resource utilization summary of the synthesized design.

## 3.9 | Remarks

The design and testing of 4 bit 4x1 mux in structural (using 4bit 2x1 mux) and RTL Verilog has been carried out. The device is showing expected behaviour.


## 4 | 4 bit 8:1 Multiplexer by instantiating 4:1, 2:1 MUXs

04-10-2023

### 4.1 | Objectives

- To design a 4 bit 8:1 Multiplexer by instantiating earlier designed multiplexers and verify its functionality using a testbench.

### 4.2 | Schematic

 

**Figure 4.1:** Block diagram of the 8x1 mux.

### 4.3 | Truth table

The truth table of the 8x1 mux:

Input 1	Input 2	Input 3	Input 4	Input 5	Input 6	Input 7	Input 8	$S_0$	$S_1$	$S_2$	Y (Output)
$A_0$	$A_1$	$A_2$	$A_3$	$A_4$	$A_5$	$A_6$	$A_7$	0	0	0	$A_0$
$A_0$	$A_1$	$A_2$	$A_3$	$A_4$	$A_5$	$A_6$	$A_7$	0	0	1	$A_1$
$A_0$	$A_1$	$A_2$	$A_3$	$A_4$	$A_5$	$A_6$	$A_7$	0	1	0	$A_2$
$A_0$	$A_1$	$A_2$	$A_3$	$A_4$	$A_5$	$A_6$	$A_7$	0	1	1	$A_3$
$A_0$	$A_1$	$A_2$	$A_3$	$A_4$	$A_5$	$A_6$	$A_7$	1	0	0	$A_4$
$A_0$	$A_1$	$A_2$	$A_3$	$A_4$	$A_5$	$A_6$	$A_7$	1	0	1	$A_5$
$A_0$	$A_1$	$A_2$	$A_3$	$A_4$	$A_5$	$A_6$	$A_7$	1	1	0	$A_6$
$A_0$	$A_1$	$A_2$	$A_3$	$A_4$	$A_5$	$A_6$	$A_7$	1	1	1	$A_7$

**Table 4.1:** Truth table for the 8x1 mux.



## 4.4 | Code

### 4.4.1 | RTL Design

```
1  `timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Company: CASEST, University of Hyderabad
4  // Author: Abhinav M
5  //
6  // Create Date: 28.09.2023 07:33:43
7  // Design Name:
8  // Module Name: BS_4_MUX81
9  // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22
23 module BS_4_MUX81(output [3:0]data, input [2:0]s, input [3:0]A0,A1,A2,A3,A4,A5,A6,A7);
24
25 wire [3:0]w1,w2;
26
27 BR_4_MUX_41 m1(w1,s[1:0],A0,A1,A2,A3);
28
29 BR_4_MUX_41 m2(w2,s[1:0],A4,A5,A6,A7);
30
31 BS_4_MUX21 m3(data,s[2],w1,w2);
32
33 endmodule
```

### 4.4.2 | Testbench

```
1  `timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Company: CASEST, University of Hyderabad
4  // Author: Abhinav M
5  //
6  // Create Date: 01.10.2023 19:00:53
7  // Design Name:
8  // Module Name: tb_BS_4_MUX81
9  // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22
23 module tb_BS_4_MUX81();
24     reg [3:0]A0,A1,A2,A3,A4,A5,A6,A7;
25     wire [3:0]data;
26     reg [2:0] s;
27     BS_4_MUX81 uut(data,s,A0,A1,A2,A3,A4,A5,A6,A7);
28
29     initial
30     begin
31
32         #10 A0=4'b0001;A1=4'b0010;A2=4'b0100;A3=4'b1000;A4=4'b1100;A5=4'b1110;A6=4'b0111;A7=4'b1111;
33         #10 s=3'b000;
34         #10 s=3'b001;
35         #10 s=3'b010;
36         #10 s=3'b011;
37         #10 s=3'b100;
38         #10 s=3'b101;
39         #10 s=3'b110;
40         #10 s=3'b111;
41
42
43     end
```




```

44     #10 $finish;
45     end
46
47
48
49 endmodule


```

## 4.5 Elaborated design

 


**Figure 4.2:** Elaborated design of the 4bit 8x1 mux using two 4bit 4x1 mux and one 4 bit 2x1 mux

## 4.6 Timing diagram

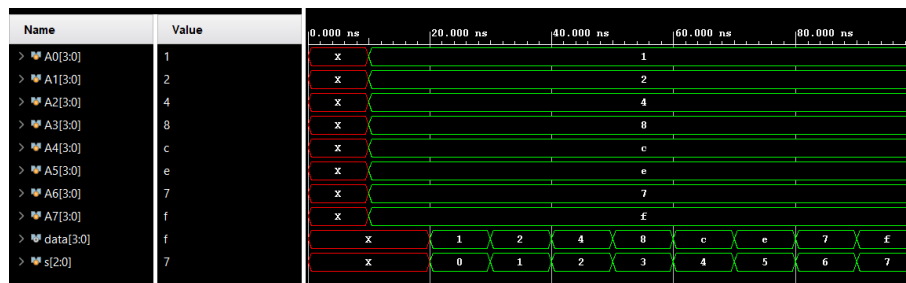

**Figure 4.3:** Timing diagram of 4bit 8x1 mux using 4x1 and 2x1 muxes.

## 4.7 Utilization summary

 

**Figure 4.4:** Utilization summary of the 4bit 8x1 mux using 4x1 and 2x1 muxes.





### 4.8 | Remarks

The design and testing of 4bit 8x1 mux using 4x1 and 2x1 muxes in structural Verilog has been carried out. The device is showing expected behaviour.

## 5 | 1 bit comparator


20-09-2023

### 5.1 | Objectives

- To design a 1 bit comparator in Structural and RTL Verilog and test its functionality.

### 5.2 | Schematic

Schematic for the 1 bit comparator is given below.

 

**Figure 5.1:** 1 bit comparator logic.

### 5.3 | Truth table

Truth table for 1 bit comparator.

A	B	LT	GT	EQ
0	0	0	0	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	1

**Table 5.1:** Truth table for a 1-bit comparator.

### 5.4 | Code

#### 5.4.1 | Structural Design

```

1  `timescale 1ns / 1ps
2  // Company: CASEST, University of Hyderabad
3  // Author: Abhinav M
4  //
5  // Create Date: 28.09.2023 07:34:41
6  // Design Name:
7  // Module Name: BS_1_comp1
8  // Project Name:
9  // Target Devices:
10 // Tool Versions:
11 // Description:
12 //
13 // Dependencies:
14 //
15 // Revision:
16 // Revision 0.01 - File Created
17 // Additional Comments:
18 //
19 //
20 //
21
22 module BS_1_comp1(output LT, EQ, GT, input a,b);
23
24 wire w1, w2;
25

```



```
26 not X1(w1, a);
27 not X2 (w2, b);
28 and X3 (LT,w1, b);
29 and X4 (GT,w2, a);
30 xnor X5 (EQ, a, b);
31
32 endmodule
```

### 5.4.2 | Testbench

```
1 `timescale 1ns / 1ps
2 ///////////////////////////////////////////////////////////////////
3 // Company: CASEST, University of Hyderabad
4 // Author: Abhinav M
5 //
6 // Create Date: 01.10.2023 17:00:37
7 // Design Name:
8 // Module Name: tb_BS_comp_1
9 // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22 module tb_BS_comp1();
23 reg a,b;
24 wire LT,EQ,GT;
25 BS_1_comp1 uut(LT, EQ, GT,a,b);
26
27 initial
28 begin
29     #5
30     a=1;b=0; #10
31     a=0;b=0; #10
32     a=0;b=1; #10
33     a=1;b=1; #10
34
35
36
37     #10 $finish;
38 end
39
40 endmodule
```

### 5.4.3 | RTL Design

```
1 `timescale 1ns / 1ps
2 ///////////////////////////////////////////////////////////////////
3 // Company: CASEST, University of Hyderabad
4 // Author: Abhinav M
5 //
6 // Create Date: 28.09.2023 07:34:55
7 // Design Name:
8 // Module Name: BR_1_comp1
9 // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22
23 module BR_1_comp1(output LT,EQ,GT, input a,b);
24
25 assign {LT, EQ, GT} = (a < b)? {1'b1, 1'b0, 1'b0} :
26                      (a==b)? {1'b0, 1'b1, 1'b0} :
27                      {1'b0, 1'b0, 1'b1};
28
```




```
29  
30 endmodule
```

## 5.4.4 | Testbench

```
1  `timescale 1ns / 1ps  
2  ///////////////////////////////////////  
3  // Company: CASEST, University of Hyderabad  
4  // Author: Abhinav M  
5  //  
6  // Create Date: 01.10.2023 22:56:09  
7  // Design Name:  
8  // Module Name: tb_BR_1_comp1  
9  // Project Name:  
10 // Target Devices:  
11 // Tool Versions:  
12 // Description:  
13 //  
14 // Dependencies:  
15 //  
16 // Revision:  
17 // Revision 0.01 - File Created  
18 // Additional Comments:  
19 //  
20 ///////////////////////////////////////  
21  
22  
23 module tb_BR_1_comp1();  
24 wire LT,EQ,GT;  
25 reg a,b;  
26 BR_1_comp1 uut(LT,EQ,GT,a,b);  
27  
28 initial  
29 begin  
30  
31     a=1;b=0;  
32     #10 a=1;b=1;  
33     #10 a=0;b=1;  
34  
35  
36  
37     #10 $finish;  
38 end  
39  
40  
41 endmodule
```

## 5.5 | Elaborated design


### 5.5.1 | Structural

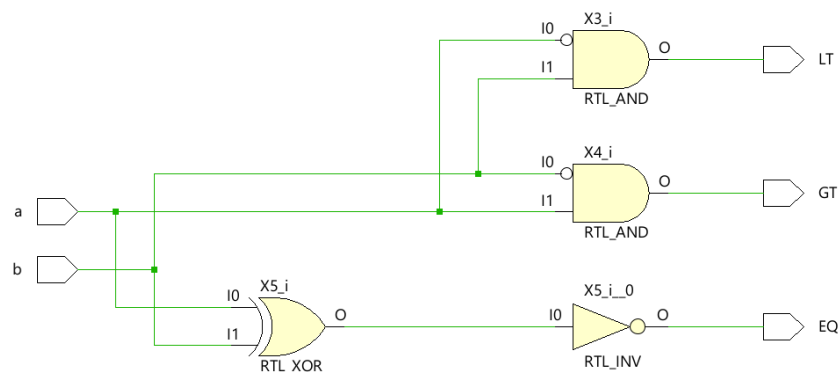

**Figure 5.2:** Elaborated design of 1 bit comparator in Structural Verilog.



### 5.5.2 | RTL

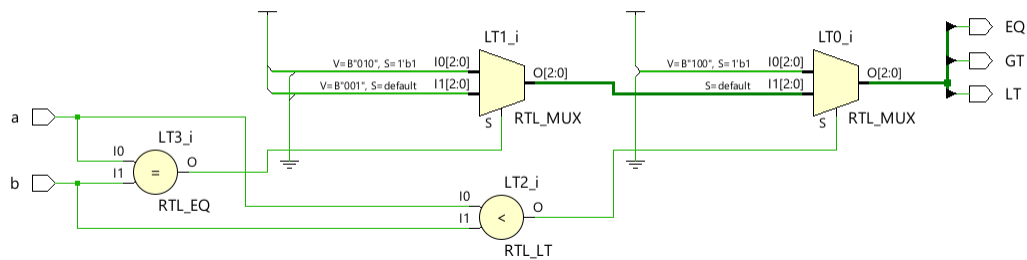

**Figure 5.3:** Elaborated design of 1 bit comparator in RTL Verilog.


## 5.6 | Timing diagram

### 5.6.1 | Structural




**Figure 5.4:** Timing diagram for 1 bit comparator in Structural Verilog.

### 5.6.2 | RTL

 


**Figure 5.5:** Timing diagram for 1 bit comparator in RTL Verilog.

## 5.7 | Utilization summary

 

**Figure 5.6:** Utilization summary of 1 bit comparator in Structural Verilog.

 

**Figure 5.7:** Utilization summary of 1 bit comparator in RTL Verilog.

## 5.8 | Remarks

The design and testing of 1 bit comparator in Structural and RTL Verilog has been carried out. The device is showing expected behaviour.

## 6 | 4 bit comparator using 1 bit comparator

20-09-2023

### 6.1 | Objectives

- To design a 4 bit comparator using 1 bit comparator in structural Verilog and test its functionality.

### 6.2 | Logic

In a 4-bit comparator, the condition of  $A > B$  can be possible in the following four cases:

1. If  $A_3 = 1$  and  $B_3 = 0$
2. If  $A_3 = B_3$  and  $A_2 = 1$  and  $B_2 = 0$
3. If  $A_3 = B_3$ ,  $A_2 = B_2$  and  $A_1 = 1$  and  $B_1 = 0$
4. If  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = B_1$  and  $A_0 = 1$  and  $B_0 = 0$

Similarly, the condition for  $A < B$  can be possible in the following four cases:

1. If  $A_3 = 0$  and  $B_3 = 1$
2. If  $A_3 = B_3$  and  $A_2 = 0$  and  $B_2 = 1$
3. If  $A_3 = B_3$ ,  $A_2 = B_2$  and  $A_1 = 0$  and  $B_1 = 1$
4. If  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = B_1$  and  $A_0 = 0$  and  $B_0 = 1$

The condition of  $A = B$  is possible only when all the individual bits of one number exactly coincide with corresponding bits of another number.

### 6.3 | Code

#### 6.3.1 | Structural Design

```
1  `timescale 1ns / 1ps
2  //////////////////////////////////////////////////
3  // Company: CASEST, University of Hyderabad
4  // Author: Abhinav M
5  //
6  // Create Date: 28.09.2023 07:35:56
7  // Design Name:
8  // Module Name: BS_4_comp4
9  // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 //////////////////////////////////////////////////
21
22 module BS_4_comp4(output LT, EQ, GT, input [3:0]a,b);
23
24 wire [3:0]LT1,EQ1,GT1;
25
26 BS_1_comp1 c0(LT1[0],EQ1[0],GT1[0],a[0],b[0]); //bit-wise comparison
27 BS_1_comp1 c1(LT1[1],EQ1[1],GT1[1],a[1],b[1]);
28 BS_1_comp1 c2(LT1[2],EQ1[2],GT1[2],a[2],b[2]);
29 BS_1_comp1 c3(LT1[3],EQ1[3],GT1[3],a[3],b[3]);
30
31 or o2(LT,LT1[3],(EQ1[3]&LT1[2]), (EQ1[3]&EQ1[2]&LT1[1]),(EQ1[3]&EQ1[2]&EQ1[1]&LT1[0])); //a<b
32
33 or o1(GT,GT1[3],(EQ1[3]&GT1[2]), (EQ1[3]&EQ1[2]&GT1[1]),(EQ1[3]&EQ1[2]&EQ1[1]&GT1[0])); //a>b
34
35 and a1(EQ,EQ1[0],EQ1[1],EQ1[2],EQ1[3]); //a==b
36
37 endmodule
38
39
```


## 6.3.2 Testbench

```

1  `timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Company: CASEST, University of Hyderabad
4  // Author: Abhinav M
5  //
6  // Create Date: 01.10.2023 16:32:12
7  // Design Name:
8  // Module Name: tb_BS_comp4
9  // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22
23 module tb_BS_comp4();
24 reg [3:0]a,b;
25 wire LT,EQ,GT;
26 BS_4_comp4 uut(LT, EQ, GT,a,b);
27 initial
28 begin
29 #5
30 a=4'b1010;b=4'b0100;#10 //g
31
32 a=4'b0010;b=4'b1100;#10 //l
33
34 a=4'b1110;b=4'b1110;#10 //e
35
36 // a=4'b1010;b=4'b0100;#10
37
38 // a=4'b0010;b=4'b1100;#10
39
40 // a=4'b1110;b=4'b1110;#10
41
42
43 #10 $finish;
44 end
45
46 endmodule

```

## 6.4 Elaborated design

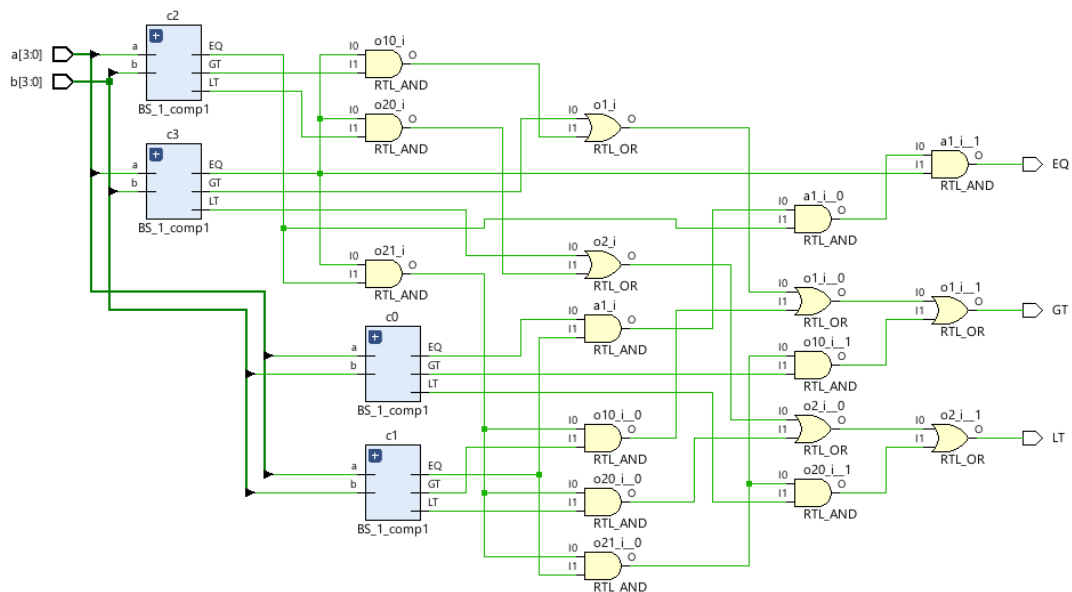


**Figure 6.1:** Elaborated design of 4 bit comparator using 1 bit comparator.






## 6.5 | Timing diagram

 

**Figure 6.2:** Timing diagram of 4 bit comparator using 1 bit comparator.

## 6.6 | Utilization summary

Resource	Utilization	Available	Utilization %
LUT	5	53200	0.01
IO	11	200	5.50

 

**Figure 6.3:** Utilization summary of 4 bit comparator using 1 bit comparator.

## 6.7 | Remarks

The design and testing of 4 bit comparator using 1 bit comparator in Verilog has been carried out. The device is showing expected behaviour.



## 7 | References



## **A | Appendix A: GitHub Repo**

The GitHub repo referenced below contains the Verilog code and testbenches mentioned in this report.

<https://github.com/AbhinavM2000/MV401D/>