

Full adder VIO

CASEST



हैदराबाद विश्वविद्यालय
University of Hyderabad

Lab Report No. 2

MV—: Digital VLSI System Design Lab

Submitted by:

Full Name	Enrollment No.
-----------	----------------

Abhinav M	23PMMT11(@uohyd.ac.in)
-----------	------------------------

Lab Instructor: Dr. Bhawna Gomber

Teaching Assistant: Mr. Piyush Kumar

Center for Advanced Studies in Electronics Science and Technology
University of Hyderabad
Hyderabad, India
May 1, 2024

Contents

1	Introduction	1
1.1	Objective	1
2	Code	1
2.1	Full adder	1
2.2	Top module	1
2.3	Testbench	2
2.4	Result	3
3	References	4
A	Appendix A: GitHub Repo	5



1 | Introduction

1.1 | Objective

Full adder implementation and verification using VIO.

2 | Code

2.1 | Full adder

```
'timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 09/13/2023 02:55:03 PM
// Design Name:
// Module Name: fa
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

module fa(
    input a,
    input b,
    input c_in,
    output s,
    output c_out
);

    wire w_1,w_2,w_3,w_4;

    xor x_1(w_1, a,b); //A XOR B
    xor x_2(s, w_1,c_in); // A XOR B XOR C_IN = SUM

    and a_1(w_3,w_1,c_in); // (A XOR B) . C_IN
    and a_2(w_4,a,b); // A.B
    or o_1(c_out,w_3); // // (A XOR B) . C_IN + AB = C_OUT

endmodule
// SUM = A XOR B XOR C_IN | C_OUT = (A XOR B) C_IN + A.B
```

2.2 | Top module



```
'timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 01/17/2024 04:25:59 PM
// Design Name:
// Module Name: top_m
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

module top_m(
    input clk
);

    wire probe_in0 ,probe_in1 ,probe_out0 ,probe_out1 ,probe_out2;

    vio_0 vio_test (
        .clk(clk),                // input wire clk
        .probe_in0(probe_in0),    // input wire [0 : 0] probe_in0
        .probe_in1(probe_in1),    // input wire [0 : 0] probe_in1
        .probe_out0(probe_out0),  // output wire [0 : 0] probe_out0
        .probe_out1(probe_out1),  // output wire [0 : 0] probe_out1
        .probe_out2(probe_out2)   // output wire [0 : 0] probe_out2
    );
    fa_ex1(probe_out0 ,probe_out1 ,probe_out2 ,probe_in1 ,probe_in0);

endmodule
```

2.3 | Testbench

```
'timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 09/13/2023 03:32:44 PM
// Design Name:
// Module Name: test_fa
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
```



```
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////
```

```
module test_fa(

    );
    reg a,b,c_in;
    wire s,c_out;
    fa uut(a,b,c_in,s,c_out);
    initial
    begin
        #10 a=0;b=0;c_in=0;
        #10 a=0;b=0;c_in=1;
        #10 a=0;b=1;c_in=0;
        #10 a=0;b=1;c_in=1;
        #10 a=1;b=0;c_in=0;
        #10 a=1;b=0;c_in=1;
        #10 a=1;b=1;c_in=0;
        #10 a=1;b=1;c_in=1;

        #10 $finish;
    end

endmodule
```

2.4 | Result

Full adder was simulated successfully and implemented in Zedboard and verified functionality with VIO.



3 | References



A | Appendix A: GitHub Repo

The GitHub repo referenced below contains the Verilog code and testbenches mentioned in this report.

<https://github.com/AbhinavM2000/MV401D/>