

Practice Questions

CASEST



हैदराबाद विश्वविद्यालय
University of Hyderabad

Lab Report No. 3

MV407: IC Design Lab-1 (Digital)

Submitted by:

Full Name	Enrollment No.
-----------	----------------

Abhinav M	23PMMT11(@uohyd.ac.in)
-----------	------------------------

Lab Instructor: Dr. Bhawna Gomber

Teaching Assistant: Ms. Bhargavi

Center for Advanced Studies in Electronics Science and Technology
University of Hyderabad
Hyderabad, India
October 10, 2023

Contents

1	Sum of Dice	1
1.1	Problem statement	1
1.2	Truth table	1
1.3	K map and Reduced Boolean expression	1
1.4	Code	1
1.5	Elaborated design	3
1.6	Timing diagram	3
1.7	Remarks	3
2	Snack Diplomacy	4
2.1	Problem statement	4
2.2	Truth table	4
2.3	K map -creamand reduced Boolean expression	4
2.4	Code	4
2.5	Elaborated design	6
2.6	Timing diagram	6
2.7	Remarks	6
3	References	7
A	Appendix A: GitHub Repo	8



1 | Sum of Dice

1.1 | Problem statement

Three dice are rolled simultaneously. For each die, let a binary signal represent whether the outcome is even or odd. Design a circuit whose output represents whether the sum of the outcomes of the three dice is even or odd. Verify its functionality using testbench.

1.2 | Truth table

The truth table can be used to derive the Boolean expression:

D_1	D_2	D_3	Y (Odd TRUE)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

1.3 | K map and Reduced Boolean expression

		D_2D_3			
		00	01	11	10
D_1	0	0	1	0	1
	1	1	0	1	0

$$Y = D_1 \oplus D_2 \oplus D_3$$

1.4 | Code

1.4.1 | Design

```
1
2 `timescale 1ns / 1ps
3
4 // Company: CASEST, University of Hyderabad
5 // Author: Abhinav M
6 //
7 // Create Date: 10/05/2023 11:58:02 AM
8 // Design Name:
9 // Module Name: three_dice
10 // Project Name:
11 // Target Devices:
12 // Tool Versions:
13 // Description:
14 //
15 // Dependencies:
16 //
17 // Revision:
18 // Revision 0.01 - File Created
19 // Additional Comments:
20 //
21
```



```
22
23
24 module three_dice(
25     output y,
26     input d1,
27     input d2,
28     input d3
29 );
30
31     assign y=d1^d2^d3;
32
33 endmodule
```

1.4.2 | Testbench

```
1
2 `timescale 1ns / 1ps
3
4 // Company: CASEST, University of Hyderabad
5 // Author: Abhinav M
6 //
7 // Create Date: 10/05/2023 12:10:38 PM
8 // Design Name:
9 // Module Name: tb_threedice
10 // Project Name:
11 // Target Devices:
12 // Tool Versions:
13 // Description:
14 //
15 // Dependencies:
16 //
17 // Revision:
18 // Revision 0.01 - File Created
19 // Additional Comments:
20 //
21 //
22
23 module tb_threedice();
24
25     reg d1,d2,d3;
26     wire y;
27
28     three_dice uut(y,d1,d2,d3);
29
30
31
32     initial
33     begin
34
35         #10 d1=0;d2=0;d3=0;
36         #10 d1=0;d2=0;d3=1;
37         #10 d1=0;d2=1;d3=0;
38         #10 d1=1;d2=0;d3=0;
39         #10 d1=1;d2=1;d3=0;
40         #10 d1=0;d2=1;d3=1;
41         #10 d1=1;d2=0;d3=1;
42         #10 d1=1;d2=1;d3=1;
43
44         #10 $finish;
45     end
46
47 endmodule
```

1.5 | Elaborated design

 


Figure 1.1: Elaborated design.

1.6 | Timing diagram

 


Figure 1.2: Timing diagram.

1.7 | Remarks

Circuit for the problem statement was designed and tested successfully.



2 | Snack Diplomacy

2.1 | Problem statement

A person “A” likes sandwich, pastry and ice-cream, person “B” likes sweetcorn and ice-cream, person “C” likes sandwich, pastry and sweetcorn. They have enough money to buy two items. Write a module which can determine, whether a choice of food items would contain at-least one food of liking for each of them. (Assign 0-1 values to each food item).

2.2 | Truth table

The truth table can be used to derive the Boolean expression:
(Let, S_a : Sandwich, S_w : Sweetcorn, I: Ice-cream, P: Pastry)

S_a	S_w	I	P	Y
0	0	1	1	1
0	1	1	0	1
1	1	0	0	1
0	1	0	1	1
1	0	1	0	1

2.3 | K map -creamand reduced Boolean expression

		IP			
		00	01	11	10
$S_a S_w$	00	0	0	1	0
	01	0	1	0	1
	11	1	0	0	0
	10	0	0	0	1

$$Y = \overline{S_a} \overline{S_w} IP + S_a \overline{S_w} I \overline{P} + \overline{S_a} S_w \overline{I} P + \overline{S_a} S_w I \overline{P} + S_a S_w \overline{I} \overline{P}$$

2.4 | Code

2.4.1 | Design

```

1
2 `timescale 1ns / 1ps
3 //////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
4 // Company: CASEST, University of Hyderabad
5 // Author: Abhinav M
6 //
7 // Create Date: 10/05/2023 12:00:18 PM
8 // Design Name:
9 // Module Name: icecream
10 // Project Name:
11 // Target Devices:
12 // Tool Versions:
13 // Description:

```



```
14 //
15 // Dependencies:
16 //
17 // Revision:
18 // Revision 0.01 - File Created
19 // Additional Comments:
20 //
21 ///////////////////////////////////////////////////
22
23
24 module icecream(output y,
25     input Sa,
26     input Sw,
27     input I,
28     input P
29 );
30
31 wire w1,w2,w3,w4,w5;
32
33 and a1(w1,Sa,Sw,~I,~P);
34 and a2(w2,~Sa,Sw,~I,P);
35 and a3(w3,~Sa,~Sw,I,P);
36 and a4(w4,~Sa,Sw,I,~P);
37 and a5(w5,Sa,~Sw,I,~P);
38
39 //assign y = (Sa)&(Sw)&(~I)&(~P) + (~Sa)&(Sw)&(~I)&(P) + (~Sa)&(~Sw)&(I)&(P) + (~Sa)&(Sw)&(I)&(~P);
40
41 or o1(y,w1,w2,w3,w4,w5);
42
43 endmodule
```

2.4.2 | Testbench

```
1
2 `timescale 1ns / 1ps
3 ///////////////////////////////////////////////////
4 // Company: CASEST, University of Hyderabad
5 // Author: Abhinav M
6 //
7 // Create Date: 10/05/2023 12:02:26 PM
8 // Design Name:
9 // Module Name: tb_icecream
10 // Project Name:
11 // Target Devices:
12 // Tool Versions:
13 // Description:
14 //
15 // Dependencies:
16 //
17 // Revision:
18 // Revision 0.01 - File Created
19 // Additional Comments:
20 //
21 ///////////////////////////////////////////////////
22
23
24 module tb_icecream();
25
26 reg Sa,Sw,I,P;
27 wire y;
28
29 icecream uut(y,Sa,Sw,I,P);
30
31 initial
32     begin
33
34         #10 Sa=1;Sw=1;I=0;P=0;
35         #10 Sa=1;Sw=0;I=1;P=0;
36         #10 Sa=0;Sw=1;I=1;P=0;
37         #10 Sa=0;Sw=0;I=1;P=1;
38         #10 Sa=0;Sw=0;I=0;P=1;
39
40
41         #10 $finish;
42     end
43
44 endmodule
```

2.5 | Elaborated design

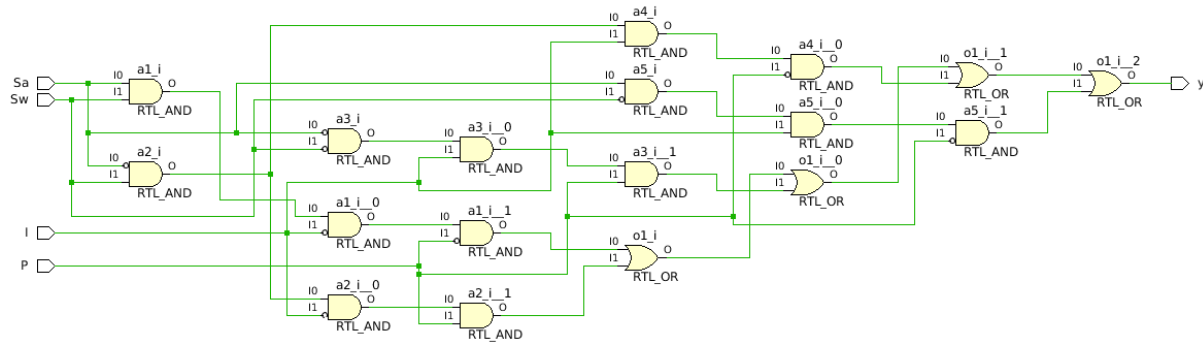


Figure 2.1: Elaborated design.

2.6 | Timing diagram



Figure 2.2: Timing diagram.

2.7 | Remarks

Circuit for the problem statement was designed and tested successfully.



3 | References



A | Appendix A: GitHub Repo

The GitHub repo referenced below contains the Verilog code and testbenches mentioned in this report.

<https://github.com/AbhinavM2000/MV401D/>