 




## Question

To design a 4- tap FIR filter, report timing, power and utilization.

## Logic



## Code

```
module tap_4_fir(  
    input [3:0] X,  
    input clk,  
    input reset,  
    output reg [10:0] out  
);  
  
    wire [3:0] H0,H1,H2,H3;  
    wire [8:0] add_out1;  
    wire [9:0] add_out2;  
    wire [10:0] add_out3;  
    wire [7:0] mul_out1,mul_out2,mul_out3,mul_out4;  
    wire [3:0] X_delay1,X_delay2,X_delay3;  
  
    // Giving h coefficient  
    assign H0 = 4'd1;  
    assign H1 = 4'd2;  
    assign H2 = 4'd3;  
    assign H3 = 4'd4;  
  
    multi m1(X,H0,mul_out1);  
    multi m2(X_delay1,H1,mul_out2);  
    multi m3(X_delay2,H2,mul_out3);  
    multi m4(X_delay3,H3,mul_out4);  
    dff d0(clk,reset,X,X_delay1);  
    dff d1(clk,reset,X_delay1,X_delay2);  
    dff d2(clk,reset,X_delay2,X_delay3);  
    addr a1(mul_out1,mul_out2,add_out1);  
    addr2 a2(add_out1,mul_out3,add_out2);  
    addr3 a3(add_out2,mul_out4,add_out3);  
  
    always @(posedge clk) begin  
        if(reset) begin
```



```
        out<= 0;
    end
    else begin
        out <= add_out3;
    end

end

endmodule

module multi (
    input [3:0] x,
    input [3:0] y,
    output [7:0] z);
    assign z = x*y;
endmodule

module addr (
    input [7:0] a,
    input [7:0] b,
    output [8:0] c);

    assign c = a + b;
endmodule

    module addr2(
        input [8:0] p,
        input [7:0] q,
        output [9:0] r);
        assign r = p + q;
    endmodule

    module addr3(
        input [9:0] a,
        input [7:0] b,
        output [10:0] c );
        assign c = a + b;
    endmodule

module dff (
    input clk,
    input reset,
    input [3:0] d,
    output reg [3:0] q
);

    always @(posedge clk) begin
        if(reset) begin
            q <= 0;
        end
        else begin
            q <= d;
        end
    end
endmodule
```



## Testbench

```

module tb1;
    reg [3:0] X;
    reg clk;
    reg reset;
    wire [10:0] out;

    tap_4_fir uut(X,clk,reset,out);

    initial begin
        clk = 1'b0;
        forever #5 clk = ~clk;
    end

    initial begin
        #5 reset = 1;
        #8 reset = 0;
        X = 4'd1;
        // #5 X = 4'd7;


        #50 $finish;
    end

end

endmodule

```

## Elaboration

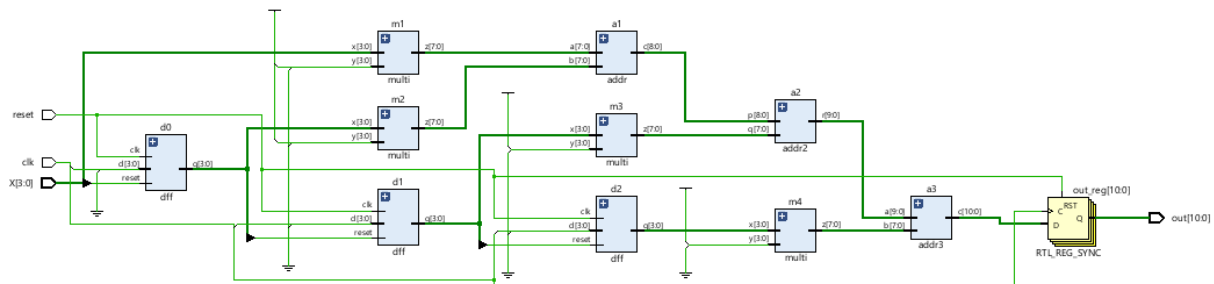

## Timing (100ns clock)

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 91.522 ns	Worst Hold Slack (WHS): 0.159 ns	Worst Pulse Width Slack (WPWS): 49.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 48	Total Number of Endpoints: 48	Total Number of Endpoints: 21

All user specified timing constraints are met.




## Power

### Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

**Total On-Chip Power:** 0.104 W  
**Design Power Budget:** Not Specified  
**Process:** typical  
**Power Budget Margin:** N/A  
**Junction Temperature:** 26.2°C  
Thermal Margin: 58.8°C (4.9 W)  
Ambient Temperature: 25.0 °C  
Effective  $\theta_{JA}$ : 11.5°C/W

### On-Chip Power

 

## Utilization

Resource	Utilization	Available	Utilization %
LUT	7	53200	0.01
FF	9	106400	0.01
IO	17	200	8.50

